



Electric circuit analysis with QuickField



**Vladimir Podnos,
Director of Marketing and Support,
Tera Analysis Ltd.**











**Alexander Lyubimtsev
Support Engineer, Tera Analysis Ltd.**



QuickField Analysis Options

Magnetic analysis suite	
Magnetic Problems	Magnetostatics
	AC Magnetics
	Transient Magnetic
Electric analysis suite	
Electric Problems	Electrostatics and DC Conduction
	AC Conduction
	Transient Electric field
Thermostructural analysis suite	
Thermal and mechanical problems	Steady-State Heat transfer
	Transient Heat transfer
	Stress analysis

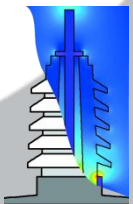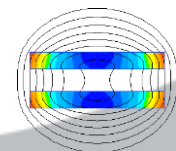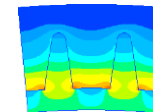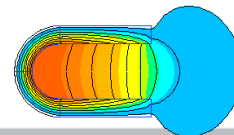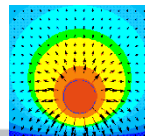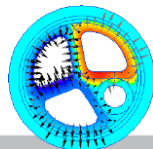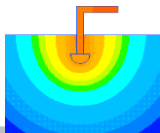
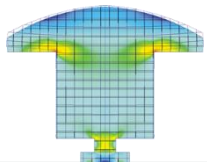




MultiPhysics.


Temperature
Field

Electromagnetic
fields

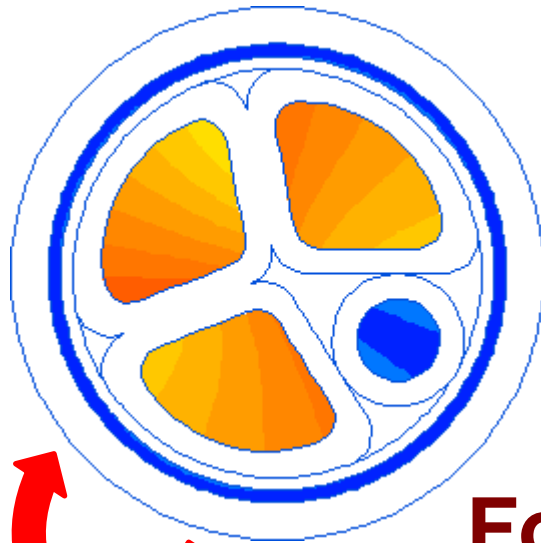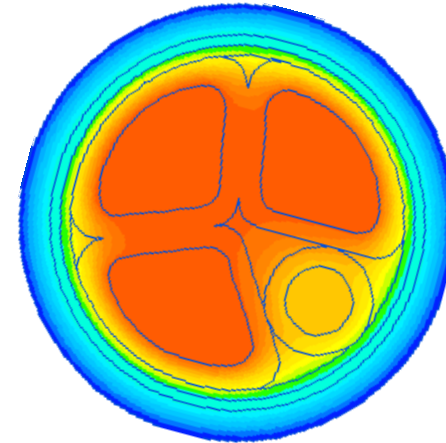

Thermal
Stresses

Forces

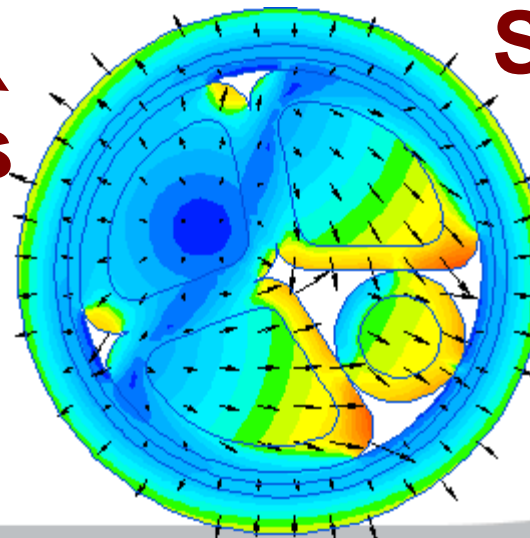









Magnetic state
import

Stresses &
Deformations




Problems with electric circuits

Magnetic analysis suite	
Magnetic Problems	Magnetostatics
	AC Magnetics
	Transient Magnetics
Electric analysis suite	
Electric Problems	Electrostatics and DC Conduction
	AC Conduction
	Transient Electric field
Thermostructural analysis suite	
Thermal and mechanical problems	Steady-State Heat transfer
	Transient Heat transfer
	Stress analysis

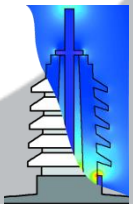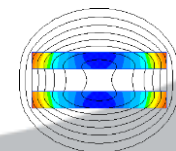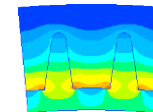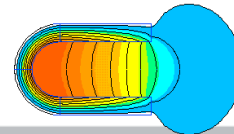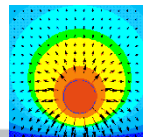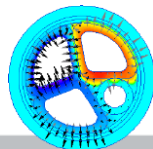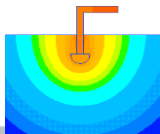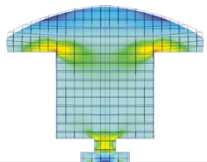




QuickField built-in circuit simulation

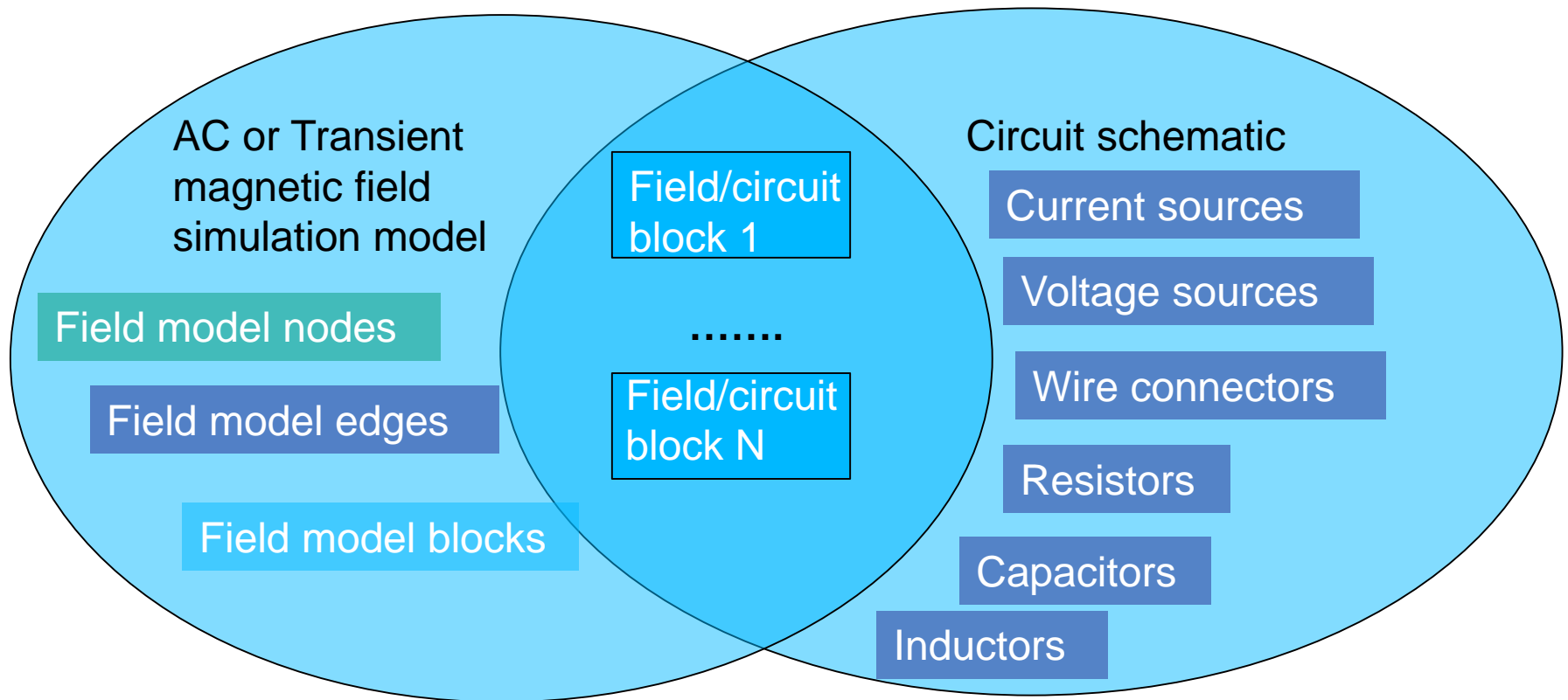




QuickField field model

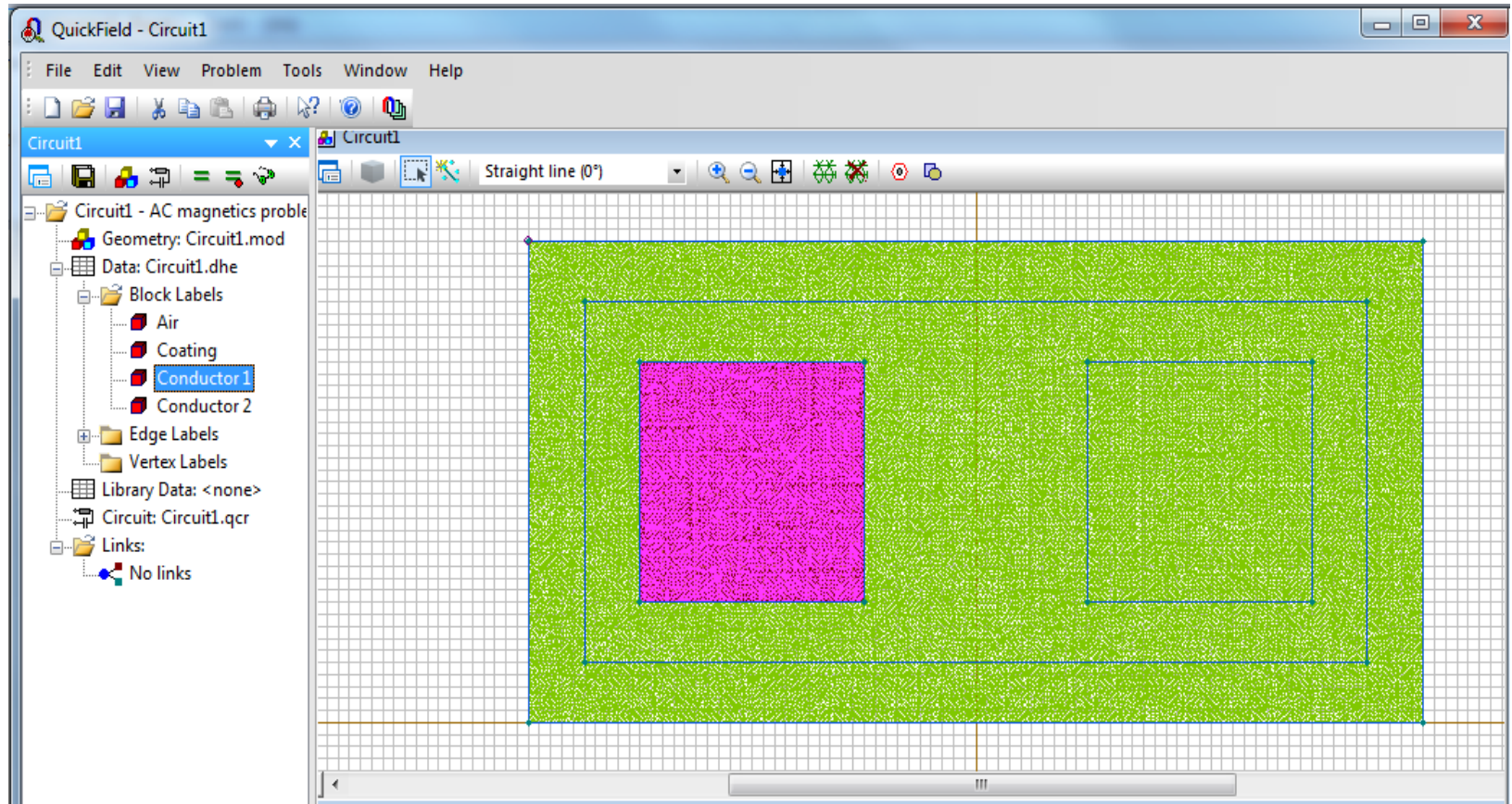




QuickField circuit elements

R C L V / Model block

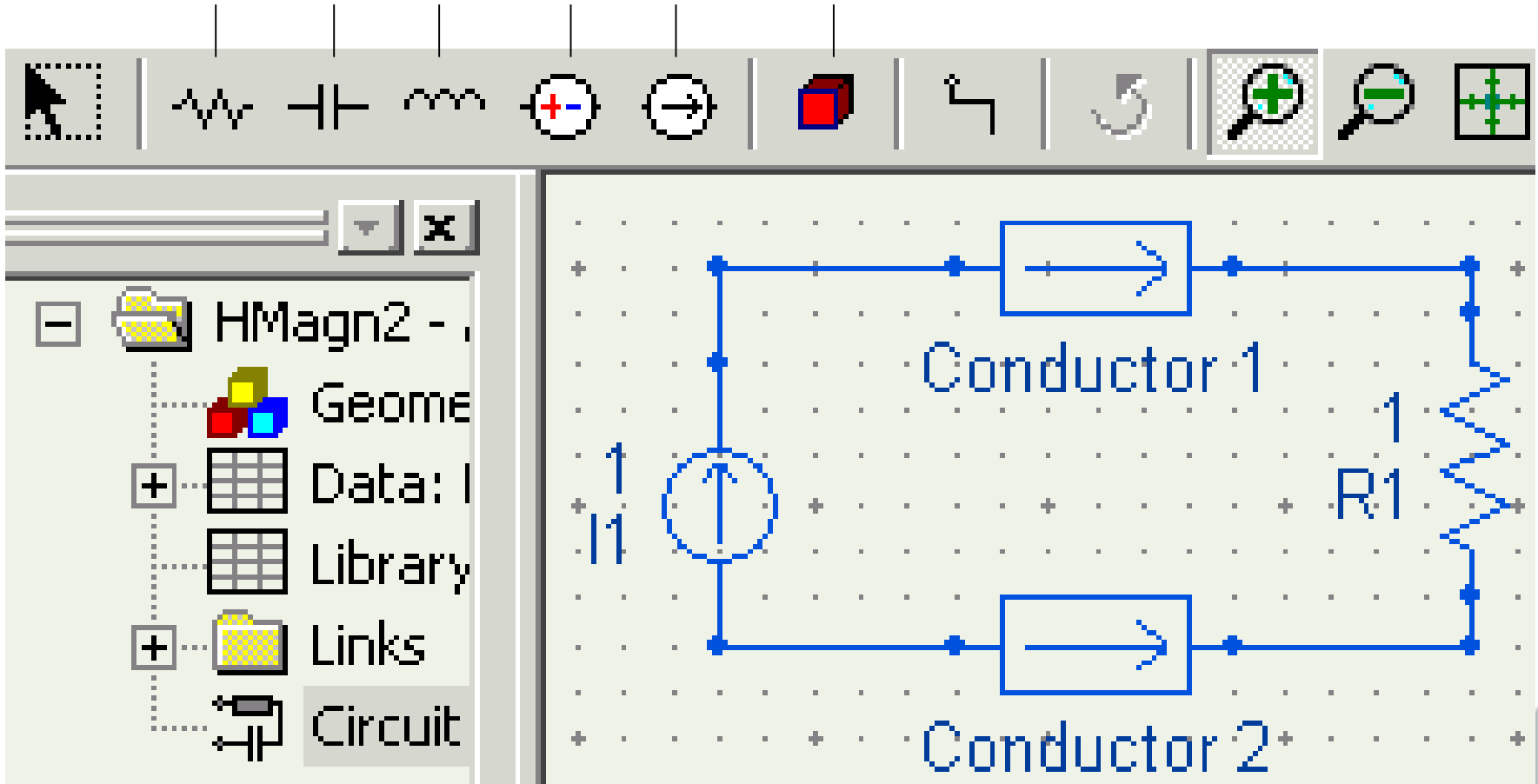


Open object interface

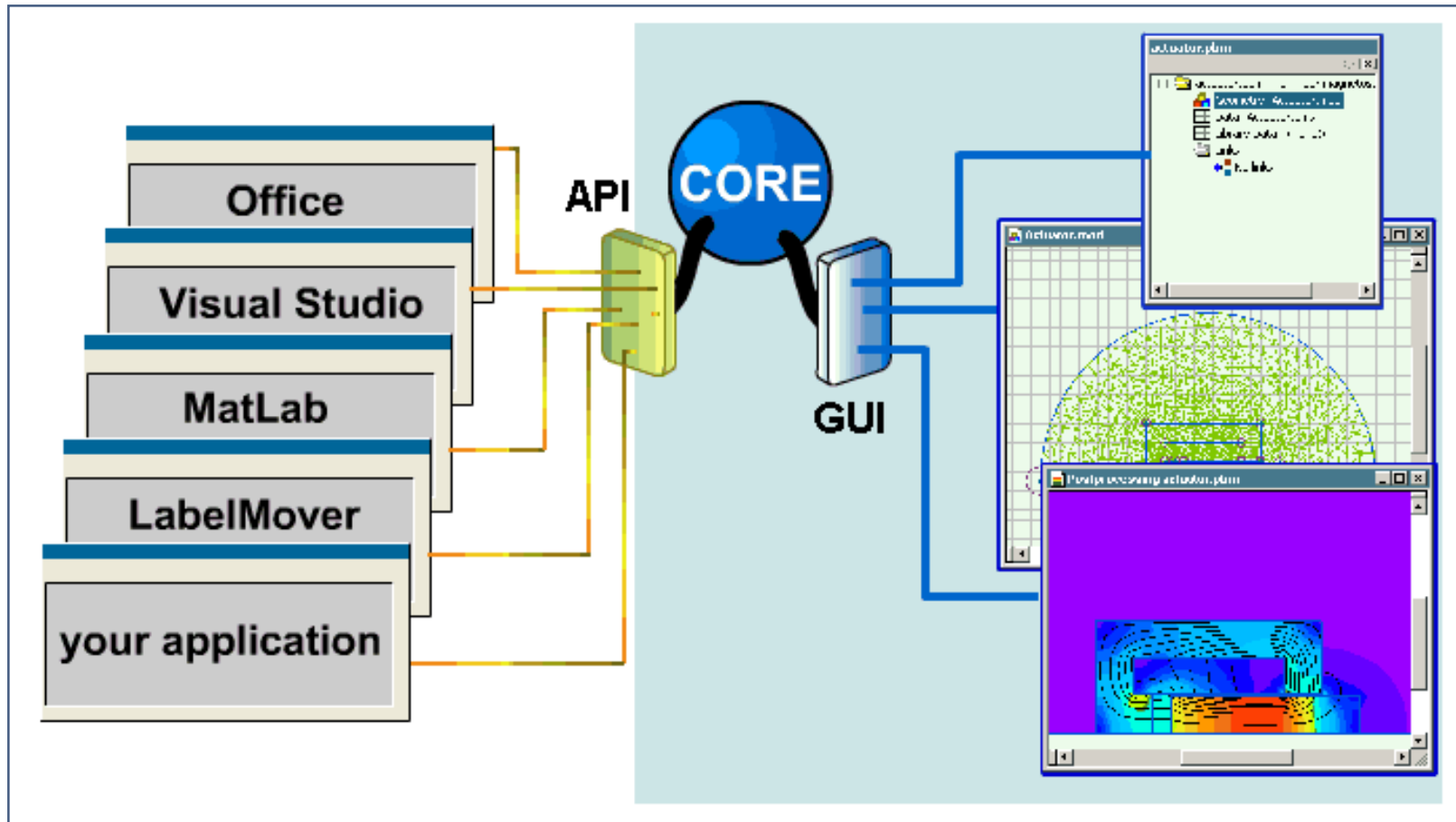




Co-simulation with Ngspice*

MS Excel VBA
application

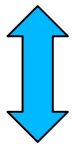

Ngspice
simulator

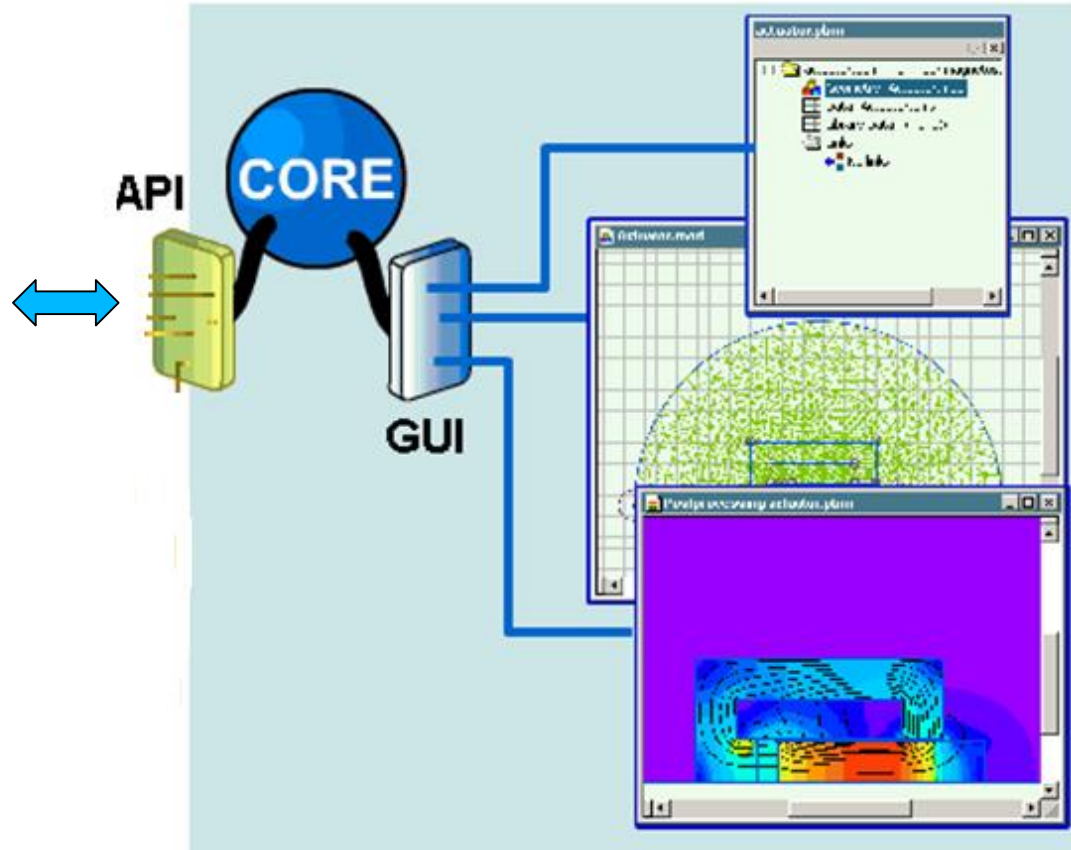

* <http://ngspice.sourceforge.net/>



QuickField Difference






Electric circuit analysis with QuickField

1. AC analysis.
2. AC frequency sweep (LabelMover tool).
3. AC analysis + field simulation (transformer).
4. Transient analysis.
5. Nonlinear circuit elements.
6. Combining QuickField with the external circuit simulator (Ngspice).



AC analysis

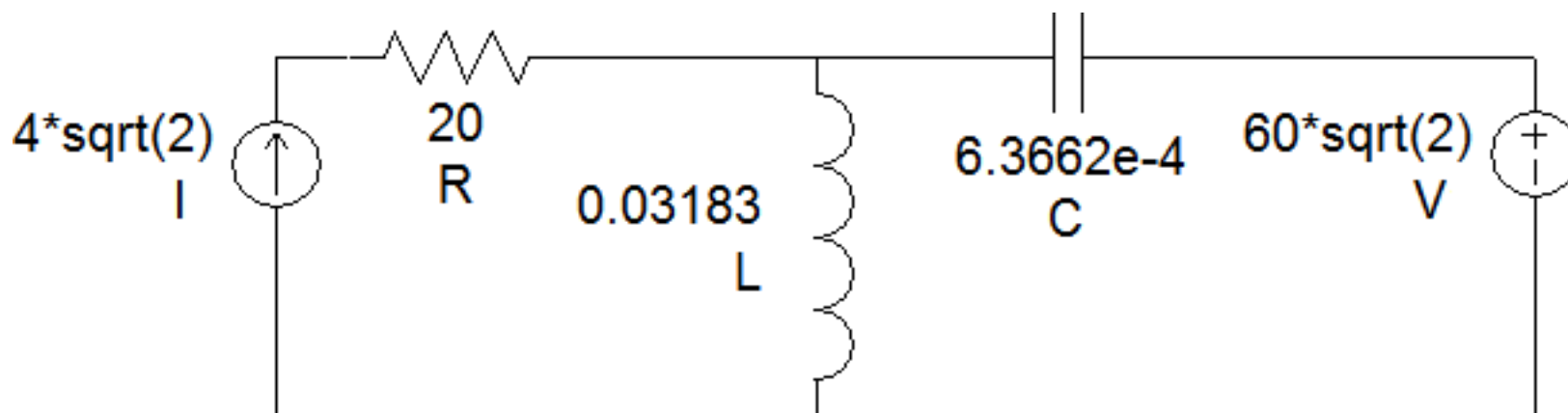

Problem specification:

Frequency $f = 50$ Hz

$X_L = 10$ Ohm

$X_C = 2$ Ohm

Current source $I = 4$ A (RMS)


Voltage source $U = 60$ V (RMS)

QuickField specific:

1. Peak values for sources
2. No fixed ground
3. Coupled field + circuit analysis



AC frequency sweep

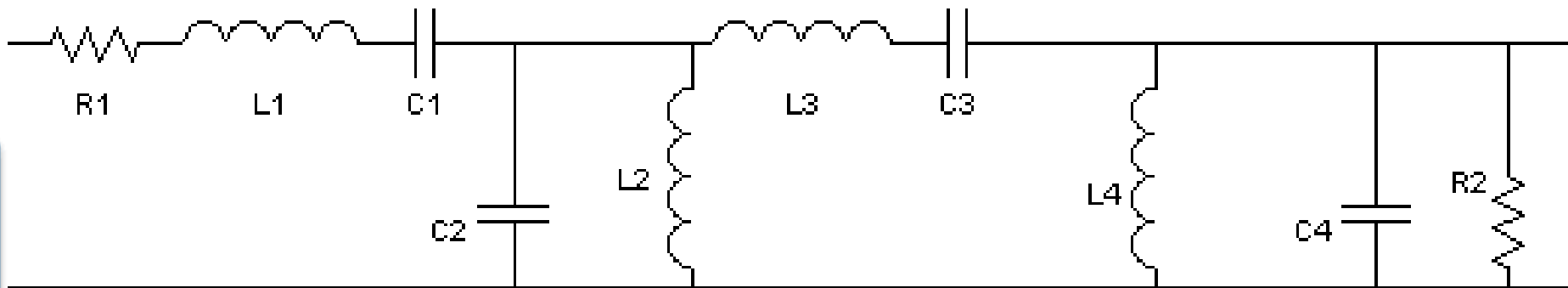

Problem specification:

$R1 = 150 \text{ Ohm}$, $R2 = 150 \text{ Ohm}$

$C1 = 840 \text{ pF}$, $C2 = 0.1637 \text{ uF}$, $C3 = 852 \text{ pF}$, $C4 = 0.0558 \text{ uF}$


$L1 = 12.11 \text{ mH}$, $L2 = 62.08 \text{ uH}$, $L3 = 11.91 \text{ mH}$, $L4 = 182.3 \text{ uH}$

Tasks:


Filter transfer function at frequency range $f = 40..60 \text{ kHz}$.



Transformer

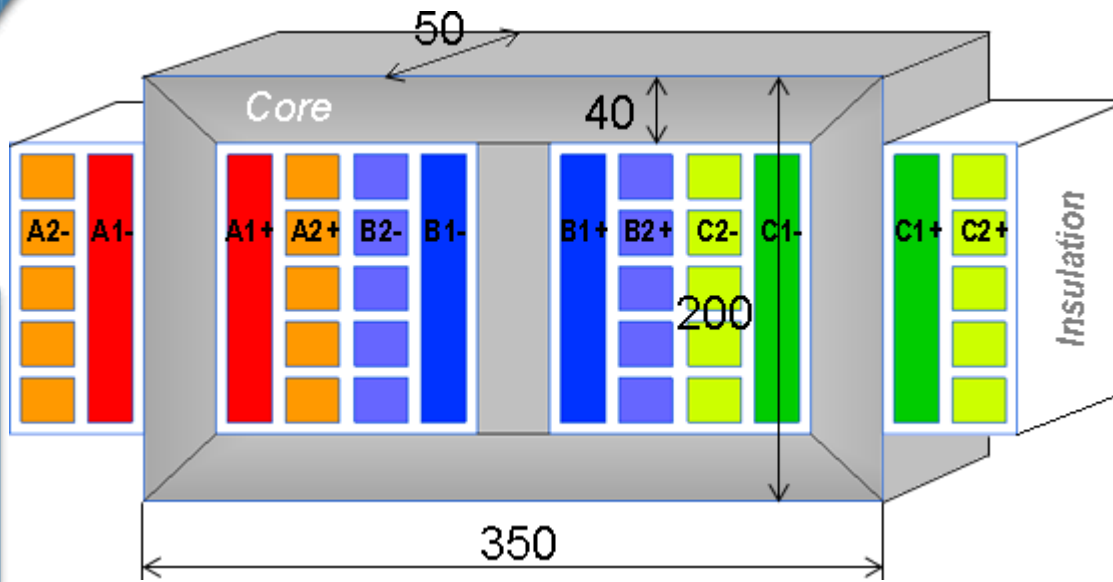

Dimensions are given in mm

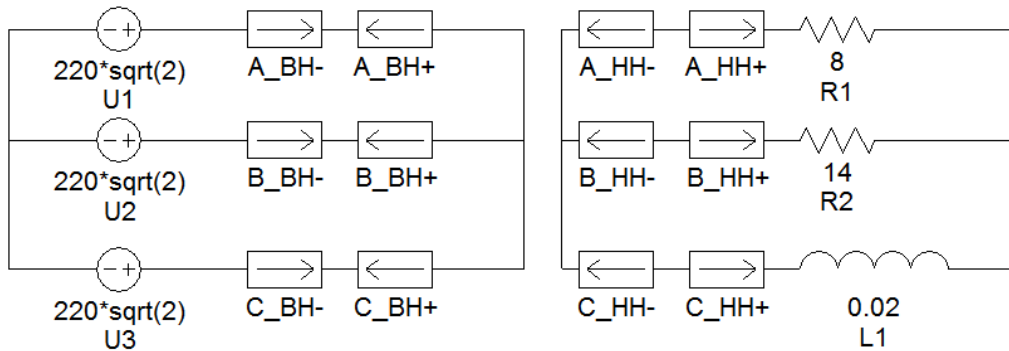

Problem specification:

Phase voltage $U = 220$ V,

Frequency $f = 50$ Hz,

Phase loads:

$$R_{1A} = 8 \Omega,$$

$$R_{2B} = 14 \Omega,$$


$$L_{1C} = 0.02 \text{ H (} 6.3 \Omega \text{)}.$$

Windings turns (Y/Y):

$$N_{LV} = 150, N_{HV} = 384.$$




Transient analysis

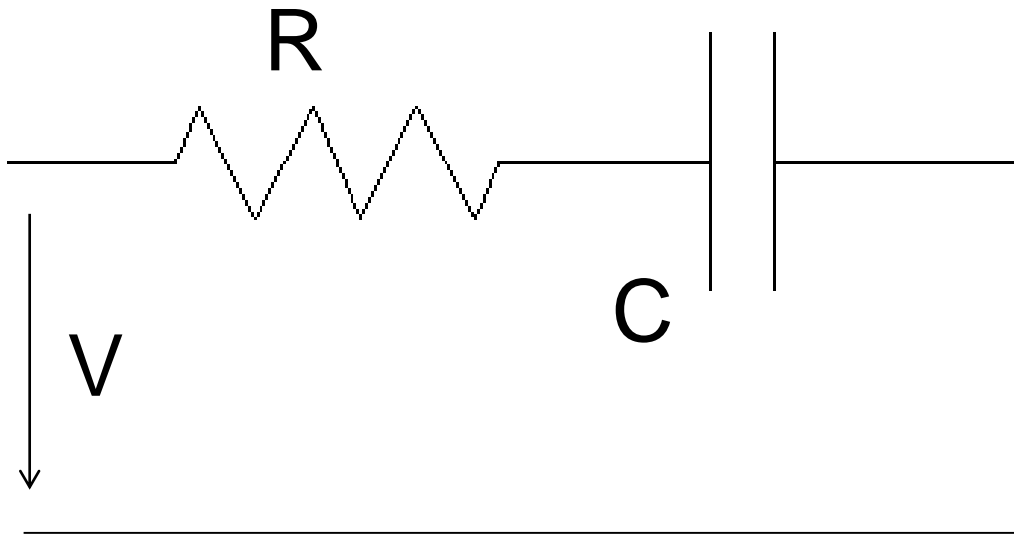

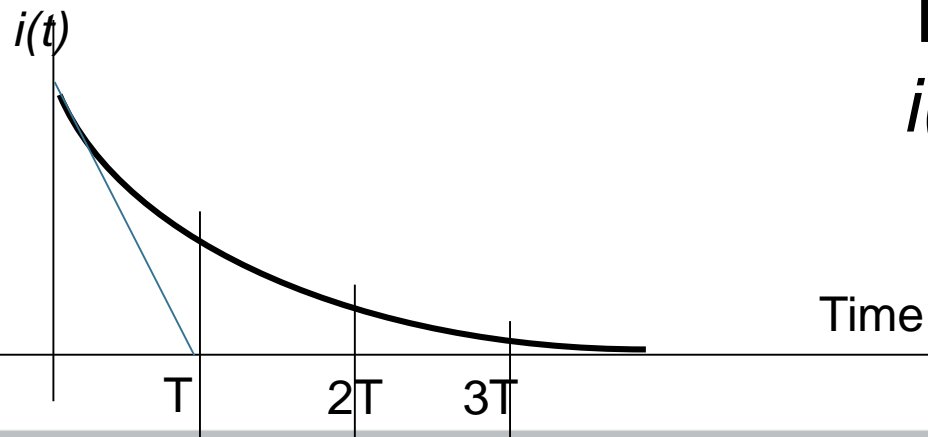Problem specification:


$R = 4.5 \text{ Ohm}$, $C = 100 \text{ uF}$.
Voltage source $V = 100 \text{ V}$



Time constant $T = C \cdot R$



$$i(t) = V/R * e^{-t/T}$$

Nonlinear elements

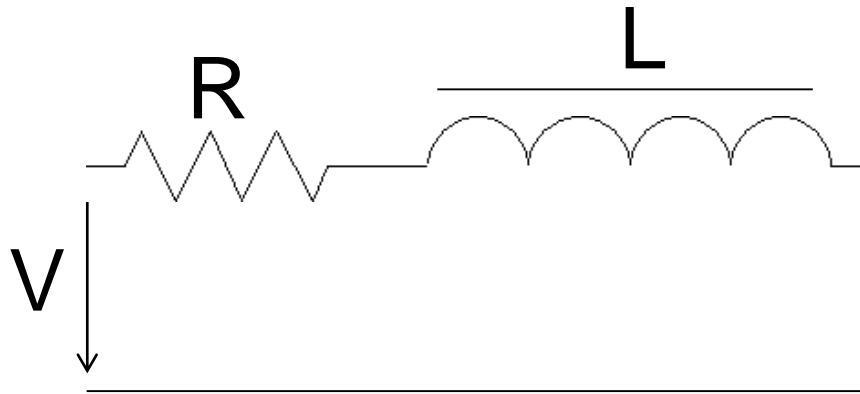

Time constant $T = L / (R + R_L)$
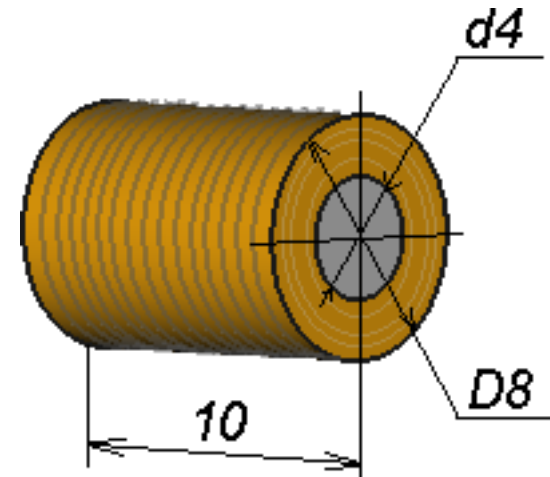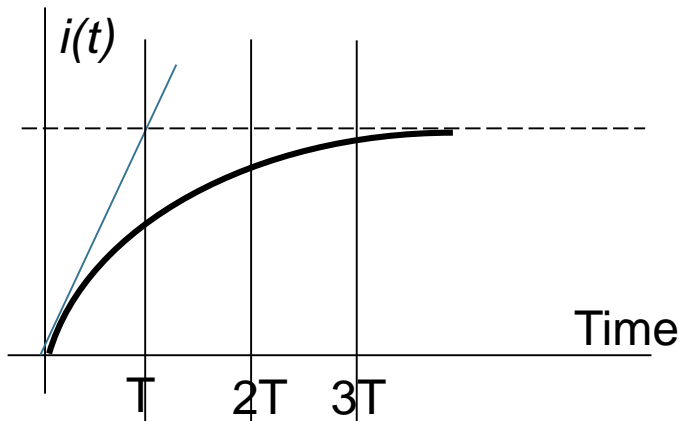
$$i(t) = V / (R + R_L) * (1 - e^{-t/T})$$





$R_L = 4.2 \text{ Ohm}$
 $L = 2.8 \text{ mH}$

Problem specification:


$R = 10 \text{ Ohm}$,
 $R_L = 4.2 \text{ Ohm}$, $L = 2.8 \text{ mH}$
Voltage source $V = 100 \text{ V}$



Co-simulation with Ngspice

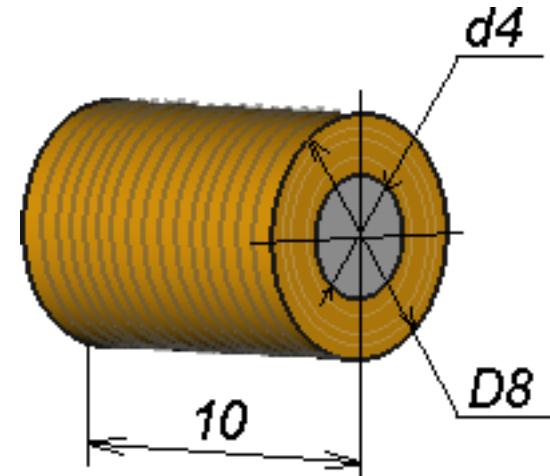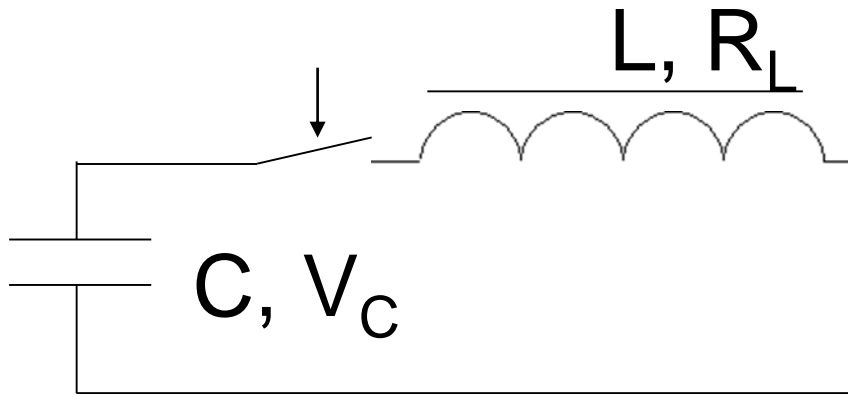
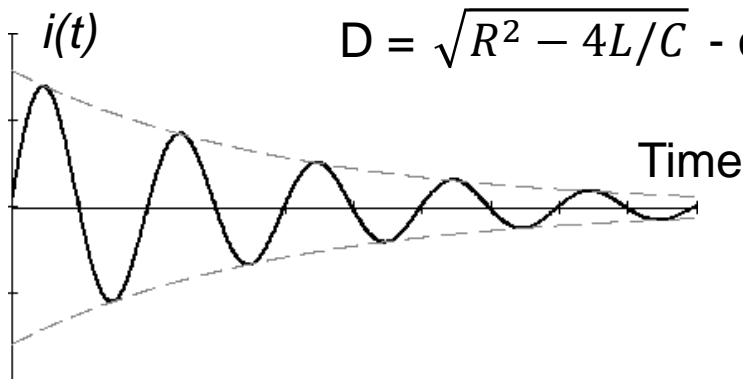
$$L \cdot di(t)/dt + R \cdot i(t) + q(t)/C = e$$



Problem specification:

$C = 100 \mu\text{F}$, $V_C = 100 \text{ V}$
 $R_L = 4.5 \text{ Ohm}$, $L = 2.5 \text{ mH}$